GaN FET-Based High CCM Totem-Pole Bridgeless PFC

Zhong Ye Alvaro Aguilar Yitzhak Bolurian Brian Daugherty



Agenda

- AC/DC efficiency standard and PFC efficiency requirement
- Bridgeless PFC topologies and development trend
- GaN (Gallium Nitride) FET overview
- Totem-pole CCM bridgeless PFC control
 - UCD3138 control implementation
 - Ideal diode emulation
 - AC crossover detection and control
- GaN device test in FET mode and diode mode
- Totem-pole CCM bridgeless PFC test
- Summary

AC/DC Efficiency Level Certifications

80 Plus Test Type	115 V Internal Non-Redundant				230 V Internal Redundant			
Fraction of rated load	10%	20%	50%	100%	10%	20%	50%	100%
80 Plus		80%	80%	80%				
80 Plus Bronze		82%	85%	82%		81%	85%	81%
80 Plus Silver		85%	88%	85%		85%	89%	85%
80 Plus Gold		87%	90%	87%		88%	92%	88%
80 Plus Platinum		90%	92%	89%		90%	94%	91%
80 Plus Titanium	90%	92%	94%	90%	90%	94%	96%	91%


Energy Star Specification


PFC Efficiency Budget

80 Plus Test Type		Efficiency at 115 V Internal Non-Redundant				Efficiency at 230 95.5%V Internal Redundant			
Fraction of rated load		10%	20%	50%	100%	10%	20%	50%	100%
80 Plus Platinum	PFC		95.8%	95.4%	93.7%		95.7%	97.4%	95.8%
	DC/DC		94%	96.5%	95%		94%	96.5%	95%
80 Plus Titanium	PFC	95.5%	95.8%	96.4%	93.8%	95.8%	98%	98.5%	94.8%
	DC/DC	94%	96%	97.5%	96%	94%	96%	97.5%	96%

- PFC design becomes more challenging at Platinum level efficiency and much harder at Titanium level efficiency
- Well designed single-phase PFC and interleaved PFC achieve around 97.5% efficiency and are just able to meet Platinum efficiency requirement
- Bridgeless seems to be the only way to reach Titanium efficiency level

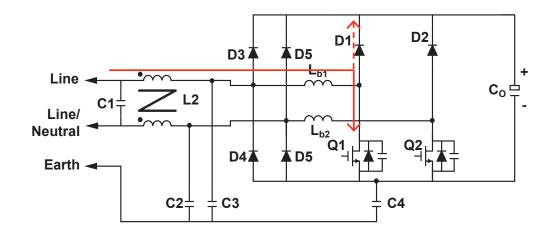Existing Bridgeless PFC Application Status



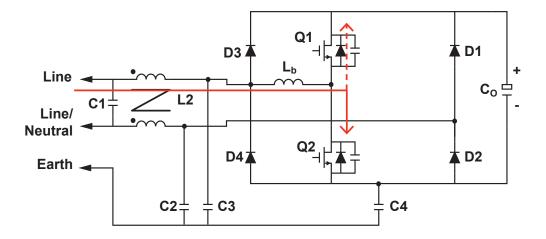

Basic Bridgeless PFC

- + Good efficiency
- + Easy control
- High component count
- Low component utilization
- Low density

Totem-Pole Bridgeless PFC

- + Good efficiency
- + Fixed frequency
- + Easy control
- DCM only
- For power < 300 W

New PFC Development Trends

Transition-Mode Totem-Pole PFC

- ZVS operation
- Interleaved configuration for high power application (around max 300 W per phase)
- Variable frequency control
- Phase shedding and adding to optimize light load efficiency
- Suitable for MOSFET applications

Continuous-Conduction-Mode Totem-Pole PFC


- Low component count
- Fixed switching frequency, zero reverse recovery switch should be used
- GaN is a good candidate for the application
- Possible to operate TM and ZVS at light loads

GaN Versus Silicon and SiC

Key electrical properties of three semiconductor materials


Properties	GaN	Si	SiC
E _G (eV)	3.4	1.12	3.2
E _{BR} (MV/cm)	3.3	0.3	3.5
V _s (x 10 ⁷ cm/s)	2.5	1.0	2.0
µ(cm²Vs)	990-2000	1500	650

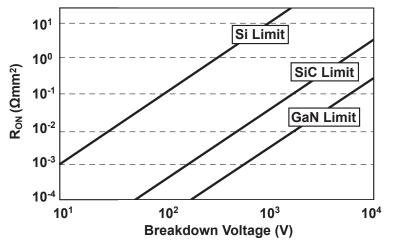Theoretical on-resistance vs blocking voltage



E_g: Wide band-gap energy

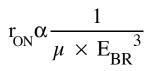- E_{BR}: Critical field break down voltage
- V_s: Saturation velocity
- **µ**: Electron mobility



Reference: EPC, Gallium Nitride (GaN) technology overview

Figure of Merit Comparison


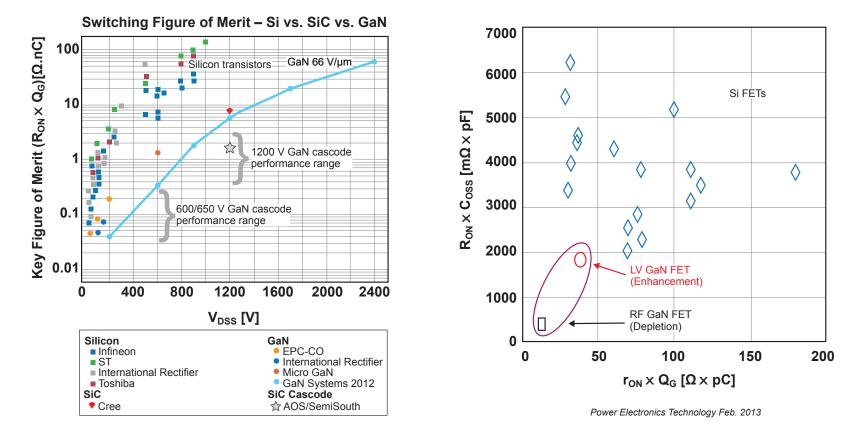


Figure of Merit depicts fundamental characteristics of switching devices – $R_{ds_{on}}$, Q_{g} , C_{OSS} and breakdown voltage

Cascode GaN FET Structure

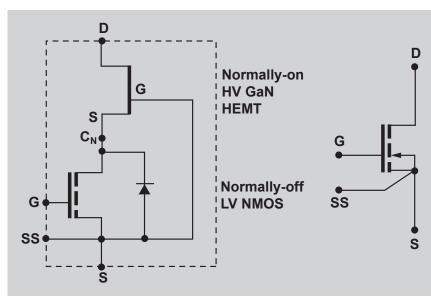


Cascode GaN FET internal structure

Advantages:

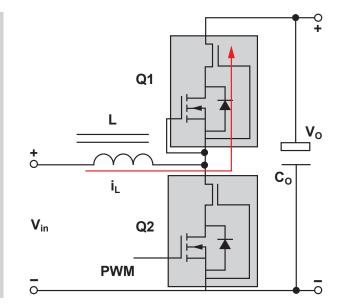- Depletion-mode GaN: low cost and better performance (compared to enhancement-mode GaN)
- Same MOSFET driver used
- Low forward voltage drop in diode mode






Example of a boost configuration

Disadvantages:

- Same reverse recovery of the cascode MOSFET body diode
- Potential MOSFET avalanche at high V_{ds} slew rate
- Large gate charge (same as the MOSFET)

Dmode-GaN + Safety FET Structure

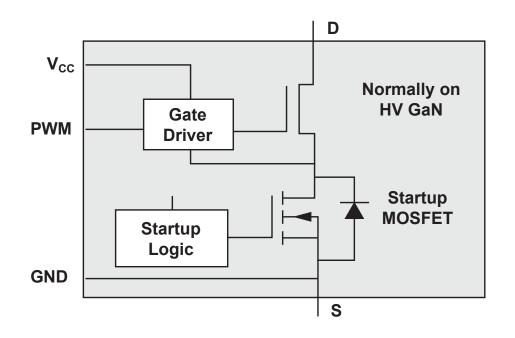


Advantages:

- Zero reverse recovery
- Low gate charge
- No LV MOSFET switching loss
- Suitable for high switching frequency applications
- Integrated gate driver circuit to ease applications

Disadvantages:


- High forward voltage drop in diode mode
- Complicated gate driver circuit (IC design)

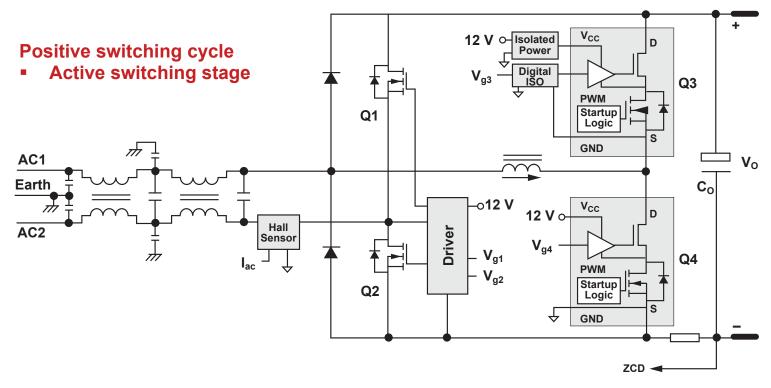GaN-Based CCM Totem-Pole Bridgeless PFC Power Stage



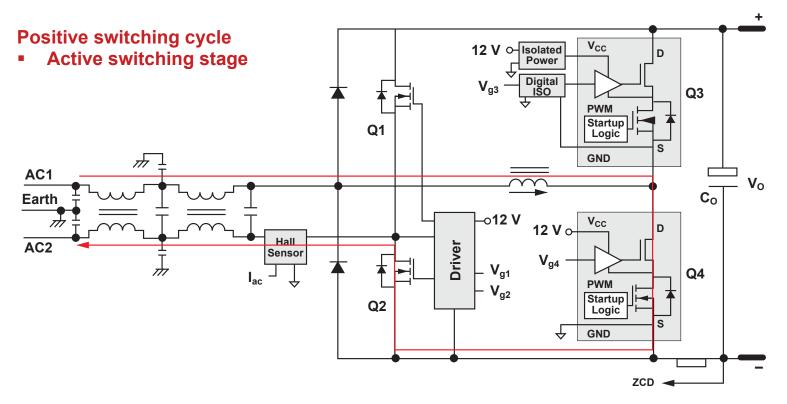
- Q1 and Q2 are low frequency switches.
- Q3 and Q4 are an active switch and a SyncFET.

GaN-Based CCM Totem-Pole Bridgeless PFC Power Stage




Positive switching cycle – active switching stage

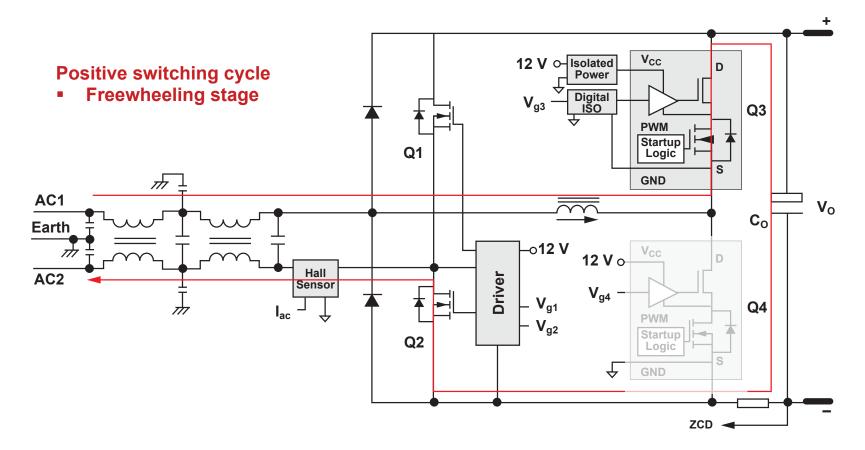GaN-Based CCM Totem-Pole Bridgeless PFC Power Stage




Positive switching cycle – freewheel stage

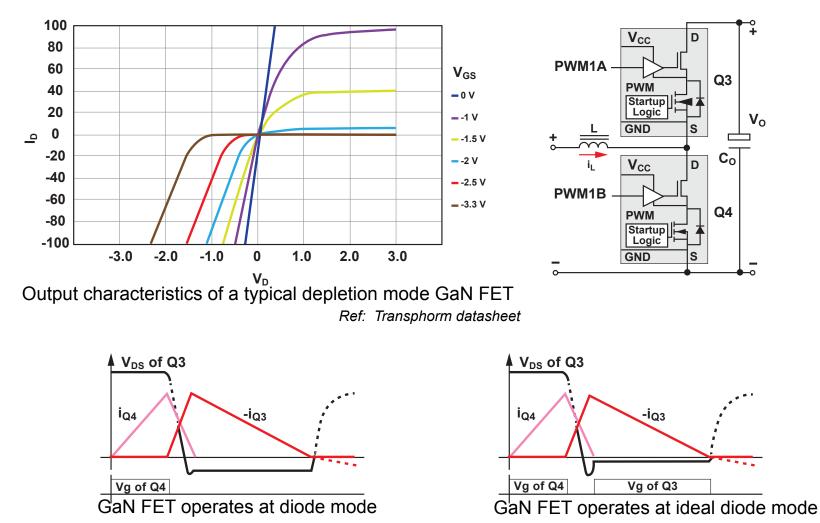
GaN FET Forward Voltage Drop and Ideal Diode Emulation Control



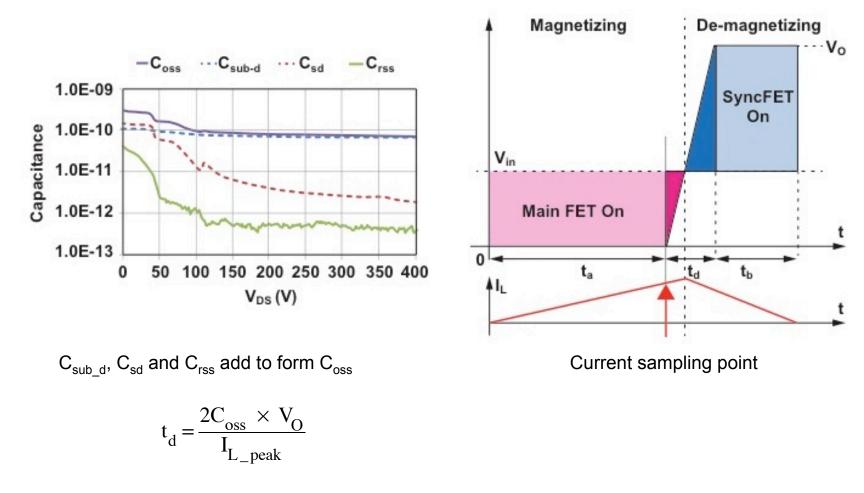
Adaptive Dead-Time Control for SyncFET to Turn On



Hardware-Assisted IDE Control

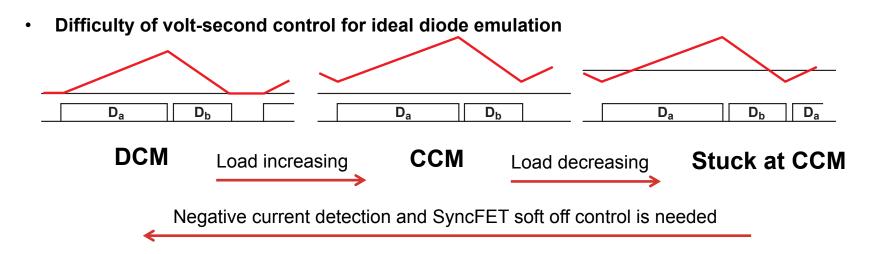


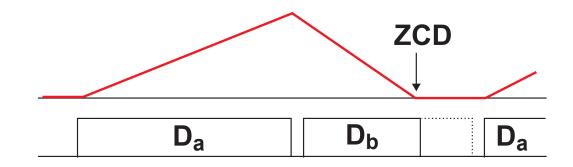• Freewheel stage current sensing for zero current detection




Db is chopped off at ZCD point

UCD3138 – Based Control Circuit

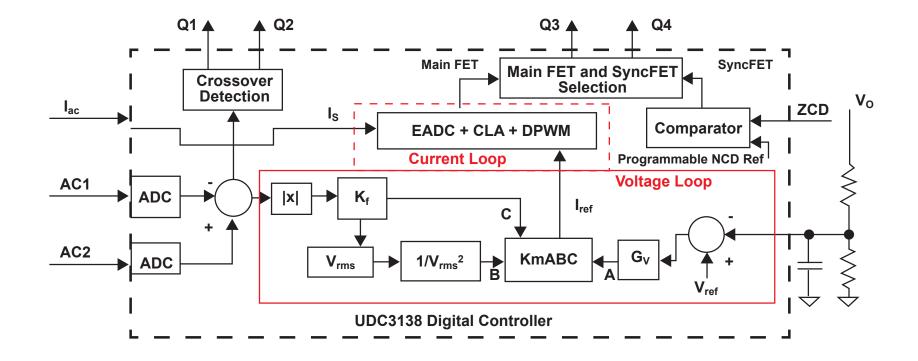

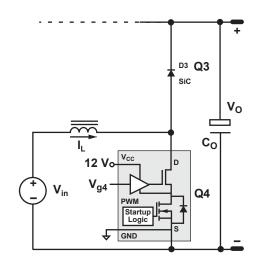Test Results – GaN FET Performance in FET Mode





Test Conditions:

- V_{in} = 200 VDC, I_{in} = 2 ADC, V_O = 400 V
- Q4: 600 V 150 m Ω depletion-mode GaN power transistor
- D3: Cree SiC diode C3D04060A
- Gate turn-off resistance = 2.2 Ω , turn-on resistance=15 Ω


Test Results:

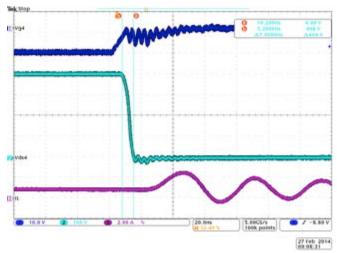- Turn-on time = 9 nS
- Max turn-on $d_V/d_t = 79 V/nS$
- Coss is linearly charged up to Vo at turn-off
- About 18 V ringing when freewheel diode conducts



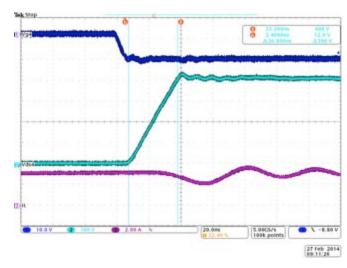

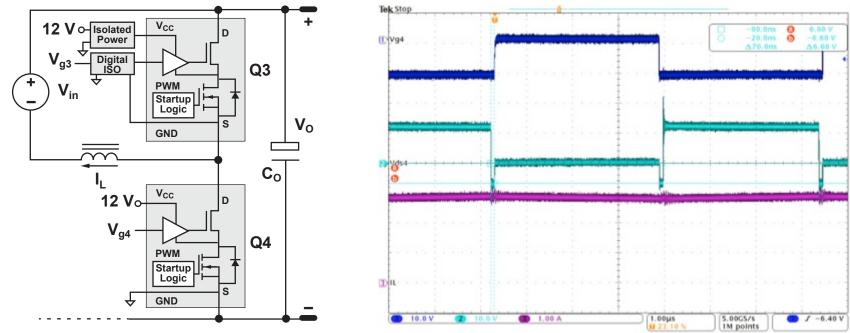Test Results – GaN FET Forward Voltage Drop in Diode Mode




Test Conditions:

• Current = 0.1 A – 3 A, dead-time = 100 nS

Test Results:


Forward voltage drop varies from 4.3 V to 7.3 V device-to-device when GaN is off

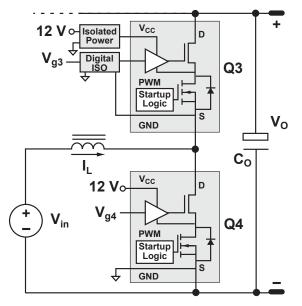Test Results – GaN FET Reverse Recovery in Diode Mode



Test Conditions:

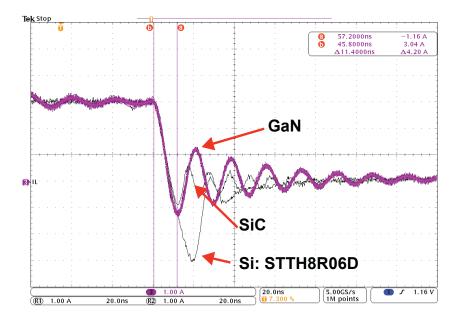
- Q3 uses GaN FET, C3D04060E and STTH8R06D
- d_i/d_t is about 368 A/µS




Test Results and Conclusions:

- Both GaN FET and SiC diode just have ringing current – no reverse current was observed
- STTH8R06D has a significant reverse current
- GaN FET has a larger ringing than SiC, but at lower frequency, as a result of larger output capacitance of the two GaN FETs

AC Current Crossover Control

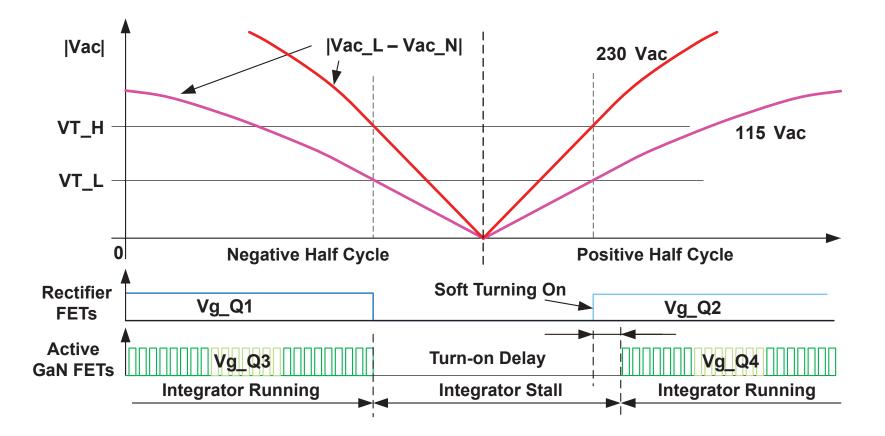


Current Spike Root Causes and Solutions

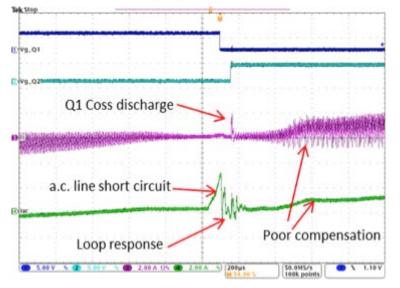

Root Causes:

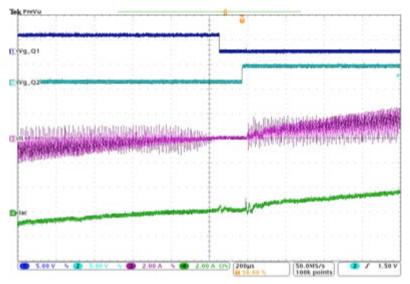
- Inaccurate a.c. voltage sensing
- Turning on rectifier FET too early cause a.c. line short sircuit
- Current loop disturbed by current spike
- Rectifier FET hard switching
- Current loop compensation not optimized




Solutions:

- Differential a.c. voltage sensing with low phase offset
- Using different a.c. crossover voltage thresholds for high line and low line
- Sufficient blanking time
- Disable PWM and stall integrator during blanking time
- Rectifier FET soft switching on
- Inserting PWM turn-on delay time
- Optimize current loop compensation

AC Current Waveforms

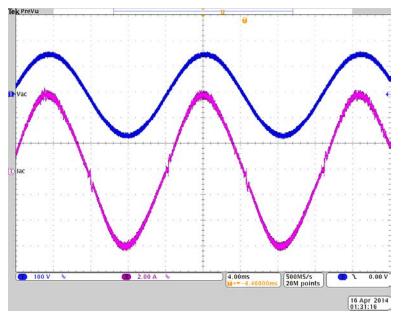


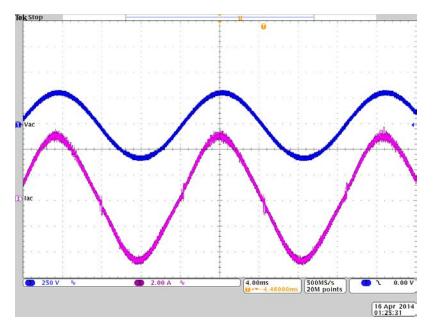115 Vac input at 450 W PF= 0.999 THD = 3.3%




230 Vac input at 750W PF= 0.995 THD = 4.0%

Totem-Pole Bridgeless PFC Efficiency

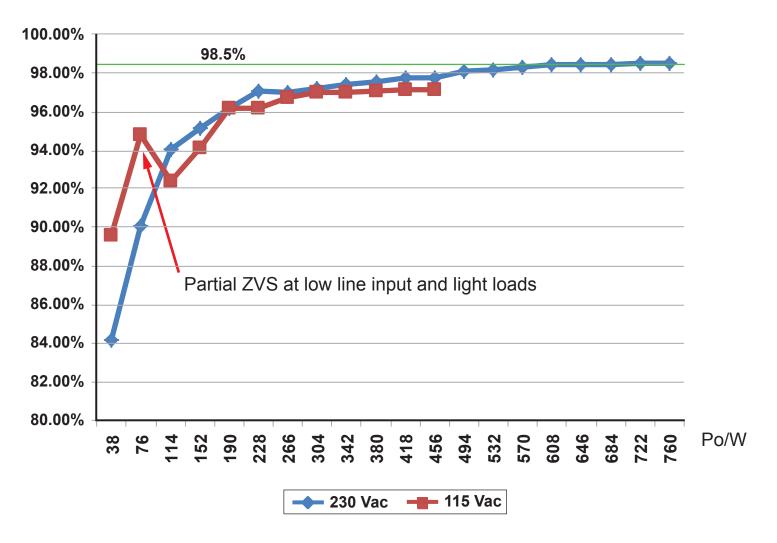

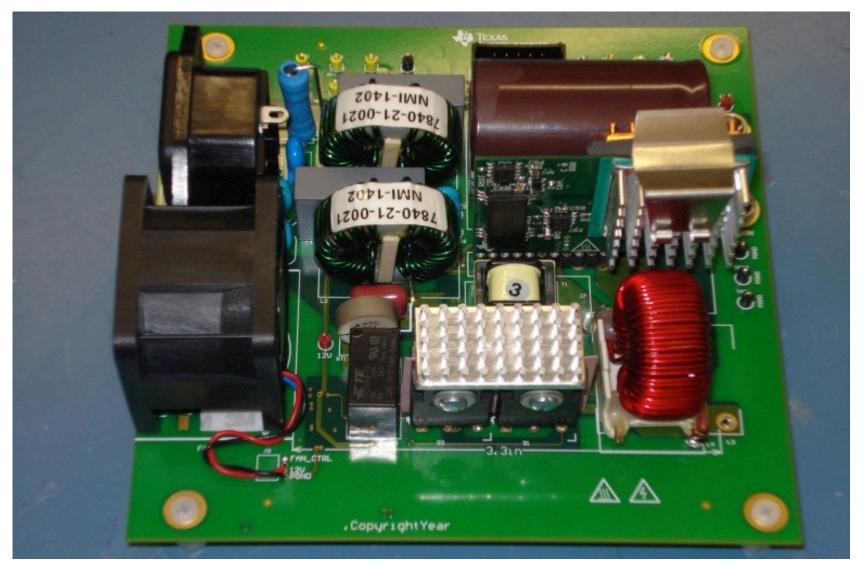750 W Totem-Pole Bridgeless PFC Prototype



Summary

- GaN FET exhibits superior switching characteristics
- Safety GaN FETs has zero reverse recovery
- Suitable for high-frequency hard-switching applications
- Relative high "body diode" forward drop
- Sophisticated ideal-diode-emulation is the key to the success of Safety GaN FET applications
- Enables Totem-Pole PFC CCM operation
- AC crossover current spike root causes were analyzed and solutions provided
- High efficiency potential
- Possible TM ZVS control to optimize light loads efficiency

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products		Applications			
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive		
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications		
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers		
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps		
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy		
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial		
Interface	interface.ti.com	Medical	www.ti.com/medical		
Logic	logic.ti.com	Security	www.ti.com/security		
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense		
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video		
RFID	www.ti-rfid.com				
OMAP Applications Processors	www.ti.com/omap	TI E2E Community	e2e.ti.com		
Wireless Connectivity	www.ti.com/wirelessconnectivity				

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2015, Texas Instruments Incorporated